

## ANALOG IC DESIGN COURSE PROJECT

Date of submission: 9/4/24

### Objectives:

Design a 2-stage Op-amp in 180 nm technology targeting different applications.

1. High Gain
2. High Gain Band Width (GBW)
3. Low area
4. Low Power

### General Specifications:

Supply voltage ( $V_{DD}$ ) = 1.8 V

Reference current source ( $I_{ref}$ ) = 20  $\mu$ A

Slew rate = 1 V/ $\mu$ s

Phase margin  $\geq 60^\circ$

Load Capacitance ( $C_L$ ) = 10 pF

ICMR = 0.6- 1.4 V

#### 1. Problem 1: High Gain

DC gain  $\geq 75$  dB

GBW  $\geq 10$  MHz

$P_{diss} \leq 1$  mW

$L_{max} \leq 2 \mu$ m

#### 2. Problem 2: High Gain Band Width (GBW)

Gain  $\geq 40$  dB

GBW  $\geq 70$  MHz

$P_{diss} \leq 1$  mW

$L_{max} \leq 2 \mu$ m

3. Problem 3: Low area(area should be minimum)

Gain  $\geq 40\text{dB}$

GBW  $\geq 10\text{MHz}$

Pdiss  $\leq 1\text{mW}$

Lmax  $\leq 2\mu\text{m}$

4. Problem 4: Low Power (Power should be minimum)

Gain  $\geq 40\text{dB}$

GBW  $\geq 10\text{MHz}$

Pdiss  $\leq 0.25\text{mW}$

Lmax  $\leq 2\mu\text{m}$

**Analysis:**

1. DC Analysis

- a. Report the schematic of the diff pair with DC OP point annotated: Id, Vgs, Vds, Vth, Vdsat, gm, gds, gmb, region.
- b. Check that all transistors operate in saturation.

2. AC Analysis.

- a. Observe pole-zero analysis of your circuit.
- b. Frequency response of your circuit.
- c. Find Av, PM, Bandwidth, CMRR, PSRR.
- d. Give a proper reason for selecting any value of any parameter.

3. Transient Analysis.

- a. slew rate.
- b. ICMR, OCMR.

EE517 Analog VLSI Lab-(Jan-May 24)-project				
Sl. No	Roll	Name	batch	Topic
1	234102406	Chandan Bordoloi	<a href="#">Batch1</a>	<a href="#">Problem1 : LM OTA : gain optimisation</a>
2	234102407	Charugundla Sai Bharath	<a href="#">Batch1</a>	
3	234102408	Deepika S	<a href="#">Batch1</a>	
4	234102409	Harsh Kumar Tiwari	<a href="#">Batch1</a>	
5	234102421	Prajakta Arvind Wakde	<a href="#">Batch2</a>	<a href="#">Problem 4: LM OTA :Power optimisation</a>
6	234102422	Saurabh kumar	<a href="#">Batch2</a>	
7	234102410	Kartali Chanukya	<a href="#">Batch2</a>	
8	234102412	Kotapati Vamshi Krishna	<a href="#">Batch2</a>	
9	234102414	Pushpendra Gurjar	<a href="#">Batch3</a>	<a href="#">Problem 3 : LM OTA:Area optimisation LM</a>
10	234102417	Soham Kundu	<a href="#">Batch3</a>	
11	234102418	Varunkumar Reddy Abbannagari	<a href="#">Batch3</a>	
12	234102419	Ameen Mohammed	<a href="#">Batch3</a>	
13	234102420	Gangala Venkata Sai	<a href="#">Batch4</a>	<a href="#">Problem 2 :OTA :bandwidth optimisation</a>
14	234102411	Kasi Viswanadham Naidu Bodepu	<a href="#">Batch4</a>	
15	234102413	Nagendra Kundrapu	<a href="#">Batch4</a>	
Total no: of students: 15				